



# Discrete Mathematics

Tutorial sheet

Boolean Algebra
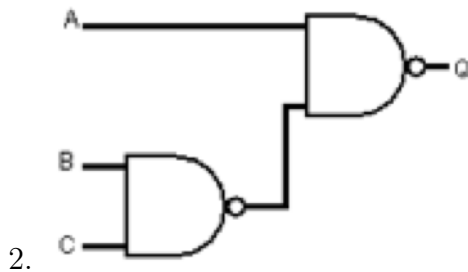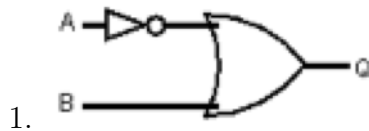
## Question 1.

What is the output for each of the following logic circuits:




Solution:

1.  $\bar{A} + B$
2.  $A(\overline{BC})$
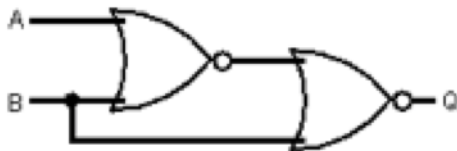
## Question 2.

Write down the truth table for the output  $Q$  of the following circuit.



Solution:

$A$	$B$	$A + B$	$\overline{A + B}$	$\overline{A + B} + B$	$Q = \overline{A + B} + B$
0	0	0	1	1	0
0	1	1	0	1	0
1	0	1	0	0	1
1	1	1	0	1	0

## Question 3.

Simplify each Boolean expression to one of the following expressions:  $0, 1, A, B, AB, A + B, \overline{AB}, \overline{A + B}, \overline{AB}$  and  $A\overline{B}$

1.  $\overline{\overline{A + B}}$
2.  $A(A + \overline{A}) + B$

$$3. (A + B)(\bar{A} + B)\bar{B}$$

Solution:

$$1. \overline{\bar{A} + \bar{B}} = A.B \text{ (De Morgan's law)}$$

$$2. A(A + \bar{A}) + B$$


$$\begin{aligned} A(A + \bar{A}) + B &= A.A + A.\bar{A} + B && \text{Distributivity} \\ &= A + 0 + B && A.A = A \text{ and } A.\bar{A} = 0 \\ &= A + B && A + 0 = A \end{aligned}$$

$$3. (A + B)(\bar{A} + B)\bar{B}$$

$$\begin{aligned} (A + B)(\bar{A} + B)\bar{B} &= (A + B)(\bar{A}.\bar{B} + B.\bar{B}) && \text{distributivity} \\ &= (A + B)(\bar{A}.\bar{B} + 0) && B.\bar{B} = 0 \\ &= (A + B)(\bar{A}.\bar{B}) \\ &= (A.\bar{A}.\bar{B} + B.\bar{A}.\bar{B}) && \text{distributivity} \\ &= (A.\bar{A}.\bar{B} + \bar{A}.B.\bar{B}) && \text{commutativity} \\ &= (0.\bar{B} + \bar{A}.0) && A\bar{A} = B.\bar{B} = 0 \\ &= (0 + 0) && 0.\bar{B} = \bar{A}.0 = 0 \\ &= 0 \end{aligned}$$

#### Question 4.

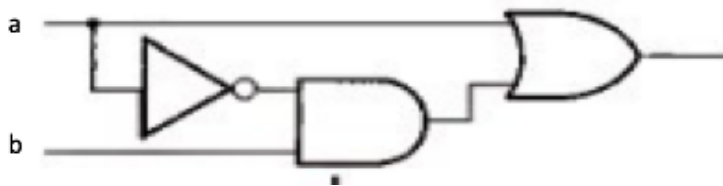1. Use the laws of boolean algebra to simplify the boolean expression:  
 $a + \bar{a}b = a + b$ .
2. Use the truth table prove that  $a + \bar{a}b = a + b$ .
3. Use the results from 1 and 2 to find a simplified circuit for the following logic circuit:




Solution:

$$\begin{aligned} a + \bar{a}b &= a.1 + \bar{a}b && \text{Identity law} \\ &= a.(1 + b) + \bar{a}b && \text{Identity law} \\ &= a.1 + ab + \bar{a}b && \text{Distributive law} \\ &= a.1 + b(a + \bar{a}) && \text{Distributive law} \\ &= a.1 + b.(1) && \text{Complement law} \\ &= a + b && \text{Identity law} \end{aligned}$$

2.

3.

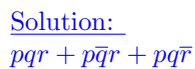1. What is the output of the following logical circuit:



- Solution:

- 2.

**Question 6.**

Use the truth table prove De Morgan's laws:  $\overline{ab} = \bar{a} + \bar{b}$  and  $\overline{a + b} = \bar{a}.\bar{b}$

Solution:

$a$	$b$	$\bar{a}$	$\bar{b}$	$a + b$	$\overline{a + b}$	$\bar{a}.\bar{b}$	$ab$	$\overline{ab}$	$\bar{a} + \bar{b}$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

The column for  $\overline{a + b}$  is the same as the column  $\bar{a}.\bar{b}$ , hence,  $\overline{a + b} = \bar{a}.\bar{b}$ .

The column for  $\overline{ab}$  is the same as the column  $\bar{a} + \bar{b}$ , hence,  $\overline{ab} = \bar{a} + \bar{b}$ .

**Question 7.**

Use the laws of boolean algebra to simplify the boolean expression:

$$\overline{ab}(\bar{a} + b)(\bar{b} + b)$$

Solution:

$$\begin{aligned}
 \overline{ab}(\bar{a} + b)(\bar{b} + b) &= \overline{ab}(\bar{a} + b).1 && \text{Complement law} \\
 &= \overline{ab}(\bar{a} + b) && \text{idempotent law} \\
 &= \bar{a}\bar{b}\bar{a} + \bar{a}\bar{b}b && \text{Distributive law} \\
 &= (\bar{a} + \bar{b})\bar{a} + (\bar{a} + \bar{b})b && \text{De Morgan's law} \\
 &= \bar{a}\bar{a} + \bar{b}\bar{a} + \bar{a}b + \bar{b}b && \text{Distributive law} \\
 &= \bar{a} + \bar{a}(\bar{b} + b) + 0 && \text{Idempotent law, Complement laws and distributive} \\
 &= \bar{a} + \bar{a}.1 + 0 && \text{complement law} \\
 &= \bar{a} + \bar{a} && \text{identity law} \\
 &= \bar{a} && \text{idempotent law}
 \end{aligned}$$

**Question 8.**

Use the laws of boolean algebra to simplify the boolean expression:

$$\bar{a}(a + b) + (b + aa)(a + \bar{b})$$

Solution:

$$\begin{aligned}
 \bar{a}(a + b) + (b + aa)(a + \bar{b}) &= \bar{a}(a + b) + (b + a)(a + \bar{b}) && \text{idempotent law} \\
 &= \bar{a}(a + b) + (a + b)(a + \bar{b}) && \text{Commutative law} \\
 &= (a + b).(\bar{a} + (a + \bar{b})) && \text{Distributive law} \\
 &= (a + b).((\bar{a} + a) + \bar{b}) && \text{Associative law} \\
 &= (a + b).(1 + \bar{b}) && \text{Complement law} \\
 &= (a + b).1 && \text{Annulment law} \\
 &= (a + b). && \text{Identity law}
 \end{aligned}$$

**Question 9.**


Prove that in a boolean algebra  $a^2 = a$ . You are required to explain your answer by making a reference to a boolean algebra axioms (laws).

Solution:

$$\begin{aligned}
 a &= a.1 && (a.1 = a) \\
 &= a.(a + \bar{a}) && (\bar{a} + a = 1) \\
 &= a.a + a.\bar{a} && (\text{distributivity of } . \text{ over } +) \\
 &= a^2 + 0 && (a.\bar{a} = 0) \\
 &= a^2 && a + 0 = a
 \end{aligned}$$
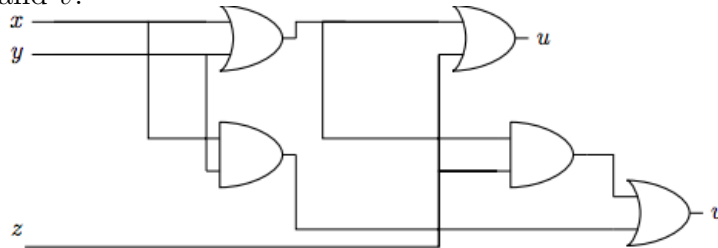
### Question 10.

The following diagram shows a circuit with three inputs and two outputs,  $u$  and  $v$ .




1. List the logic gates used in this circuit.
2. Describe each output  $u$  and  $v$  as a Boolean expression in terms of  $x$ ,  $y$  and  $z$ .

Solution:

1. 2 and-gates and 3 or-gates
2.  $u = x + y + z$  where as  $v = ((x + y).z) + (x.y) = x.y + x.z + y.z$
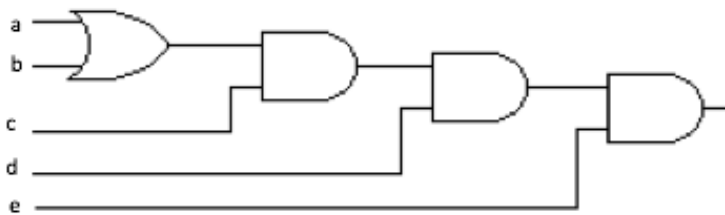
### Question 11.

Derive the Boolean expression for the following logic circuit shown below



Solution:

$$(a+b).c.d.e$$

### Question 12.

1. Write down a boolean expression for the following input/output behaviour.


x	y	z	u
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

- Construct the corresponding circuit of the above expression using not-gates, and-gates and or-gates only.

Solution:

- In order to answer this questions we need to check all combination that makes the output 1 the and-gates then use or-gates to link all the possible true outputs. by doing this we will get:
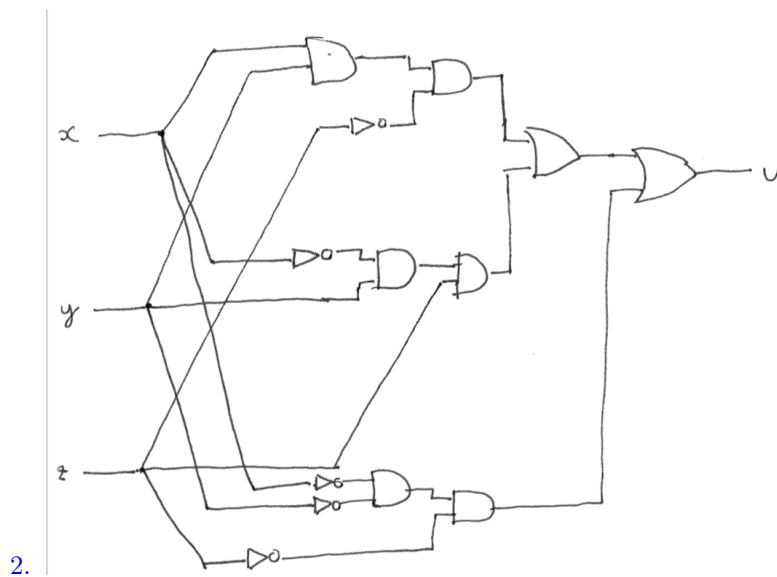
$$u = (x.y.\bar{z}) + (\bar{x}.y.z) + (\bar{x}.\bar{y}.\bar{z}).$$




### Question 13.

Given the following boolean expression  $\overline{\overline{(x + y)} + \bar{z}}$ .


- Construct its corresponding circuit.
- Use DeMorgan's laws to find a simpler form for this expression
- Construct the circuit the simplified expression.

Solution:

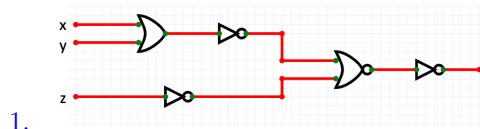

1.

2.  $(x + y)z$

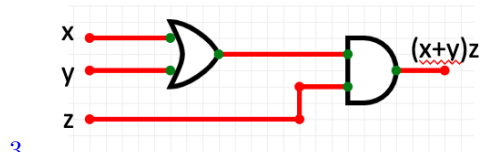

3.

### Question 14.

Simplifying the following boolean expression using Karnaugh Map

$$\bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + ab\bar{c}$$

Solution:

c \ ab	00	01	11	10
0	1	1	1	
1		1		

We can now group the 1's as follows:

c \ ab	00	01	11	10
0	1	1	1	
1		1		

Now for each grouping, we are not going to consider any variable that is changing.

For the first grouping in yellow, consists of two 1's which correspond to  $a = 0, b = 0, c = 0$  and  $a = 0, b = 1, c = 0$ . In another way, the value in this first grouping is independent from the value of  $b$ . so when  $a = 0$  and  $c = 0$  the output is 1. hence, this can be reduced to just  $\bar{a}\bar{c}$

For the green grouping which consists of two 1's corresponding to  $a = 0, b = 1, c = 0$  and  $a = 0, b = 1, c = 1$ . In another way, the value in this first grouping is independent from the value of  $c$ . so when  $a = 0$  and  $b = 1$  the output is 1. hence this can be reduced to  $\bar{a}b$

Finally, for the second grouping in orange consists of two 1's which correspond to  $a = 0, b = 1, c = 0$  and  $a = 1, b = 1, c = 0$ . In another way, the value in this first grouping is independent from the value of  $a$ . so when  $b = 1$  and  $c = 0$  the output is 1. Hence this can be reduced to just  $b\bar{c}$ .

The final reduced expression is then  $\bar{a}\bar{c} + \bar{a}b + b\bar{c}$

**Question 15.**

Given the following boolean function

$$f(a, b, c, d) = \bar{a}\bar{b}cd + \bar{a}bcd + abcd + \bar{a}bcd + ab\bar{c}\bar{d} + ab\bar{c}d + abc\bar{c}$$

1. Fill in the missing value in the following Karnaugh map of  $f(a, b, c)$ :

ab \ cd	00	01	11	10
00				
01				
11				
10				

2. Use K-map in (1) to find the minimum sum of products of  $f(a, b, c)$ .

Solution:

1.

ab \ cd	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	1	1	1	1
10	0	0	1	0

ab \ cd	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	1	1	1	1
10	0	0	1	0


- 2.

Hence,  $f(a, b, c) = ab + cd$ .

**Question 16.**

Given the following circuit:



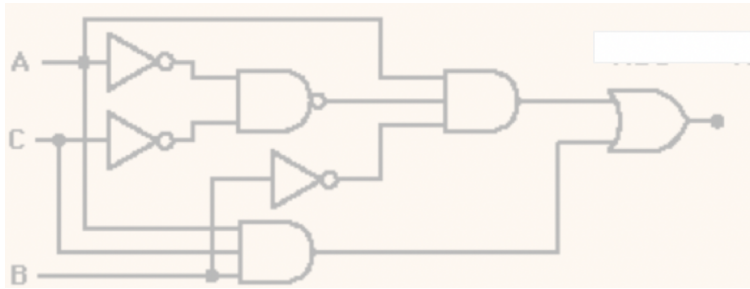

1. Find the output of this circuit.
2. Use the laws of algebra to give a simpler expression for this output.
3. Use the result in 2 to draw a simpler circuit equivalent circuit.

Solution:

$$1. ABC + AB(\overline{AC})$$

$$\begin{aligned}
 ABC + AB(\overline{AC}) &= ABC + AB(\overline{A} + \overline{C}) && \text{De Morgan's law} \\
 &= ABC + AB\overline{A} + AB\overline{C} && \text{Distributive law} \\
 &= ABC + A\overline{B}A + AB\overline{C} && \text{Complement law} \\
 &= ACB + AA\overline{B} + AC\overline{B} && \text{Associative law} \\
 &= ACB + AB + AC\overline{B} && \text{Idempotent law} \\
 &= AC(B + \overline{B}) + AB && \text{Idempotent law} \\
 &= AC.(1) + AB && \text{Complement law} \\
 &= AC + AB && \text{Identity law} \\
 &= A(C + \overline{B}) && \text{Identity law}
 \end{aligned}$$

$$3. ABC + AB(\overline{AC}) = A(C + \overline{B}), \text{ hence the simplified circuit is :}$$




### Question 17.

A set of three sensors in a factory detects whether the pollution level it is outputting from an incinerator exceeds the safety limit. In which case the incinerator is shut down. An alarm  $A$  goes off if at least two the three sensors  $s_1, s_2$  and  $s_3$  detect a pollution level above the limit. Draw a logic circuit for the system showing the inputs  $s_1, s_2$  and  $s_3$  and the output  $A$ .

Solution:

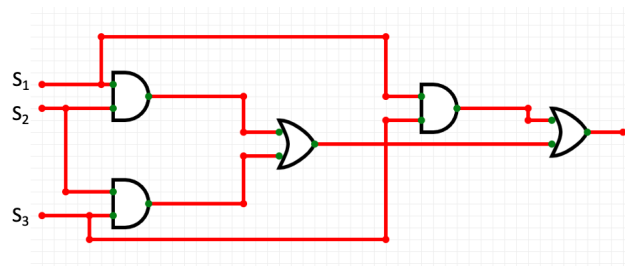The output of this circuit should be  $A = s_1.s_2 + s_1.s_3 + s_2.s_3$ . The logical circuit for the output  $A$  is



End of questions